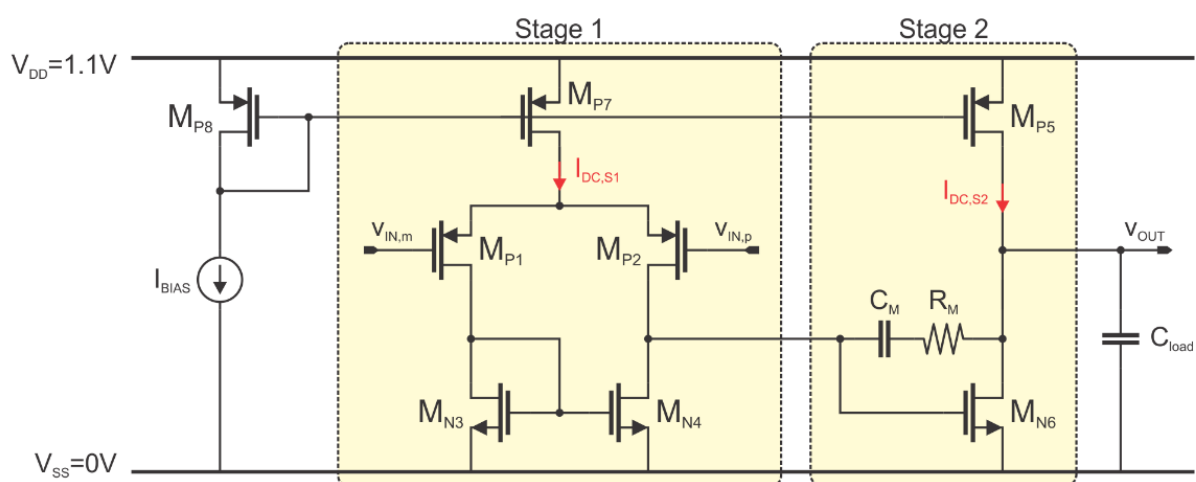


**Analog Electronic Circuits – 2021-2022**  
**Design Project Report**

**Group data**

Group number	
Name – Student 1	Semilogo Ogungbure
Name – Student 2	

**Goal:**



Design of the 2stage OpAmp such that it passes the given specifications (insert your specs below):

$C_{load} [pF]$	3
DC gain [dB]	48
$f_{GBW} [MHz]$	50
Phase margin (PM) [deg]	> 70
Output swing [V]	> 0.7

**Plan: Design of the 2-stage OpAmp on paper (10 points)**

- 1) Calculate the  $V_{OV}$ ,  $g_m$ ,  $I_{DS}$  and  $L$  of each transistor (see exceptions under “Remark”) and the required  $C_M$  and  $R_M$  in the OpAmp circuit. For that, insert all your calculations as well as your  $\frac{g_m}{g_{ds}}$ ,  $\frac{g_m}{I_D}$ -plots you used for your handcalculations below:

Hints:

- First, plot  $\frac{g_m}{g_{ds}}$  and  $\frac{g_m}{I_D}$  across  $V_{OV}$  and gatelength  $L$  and do it again across  $V_{GS}$ , as presented in the 1<sup>st</sup> session. Think about whether to create the plots for a PMOS or for a NMOS device.
- Then, based on those plots, start your calculations.
- Furthermore, you can assume the following:  
 (1) the OpAmp is designed in triple-well-technology (i.e.  $V_{SB} = 0$ ); (2)  $V_{dsat} \approx V_{OV}$  and  $V_{dsat} \geq 50\text{mV}$  across  $V_{OV}$ ; (3)  $C_M = \frac{1}{4} \cdot C_L$

Remarks:

- For Mp5, Mp7 and Mp8 you are not required to calculate the  $g_m$

Plots used for the handcalculations:

 


Fig.1

**Figure 1:**  $\frac{g_m}{g_{ds}}$  vs  $V_{OV}$  across gatelength  $L$

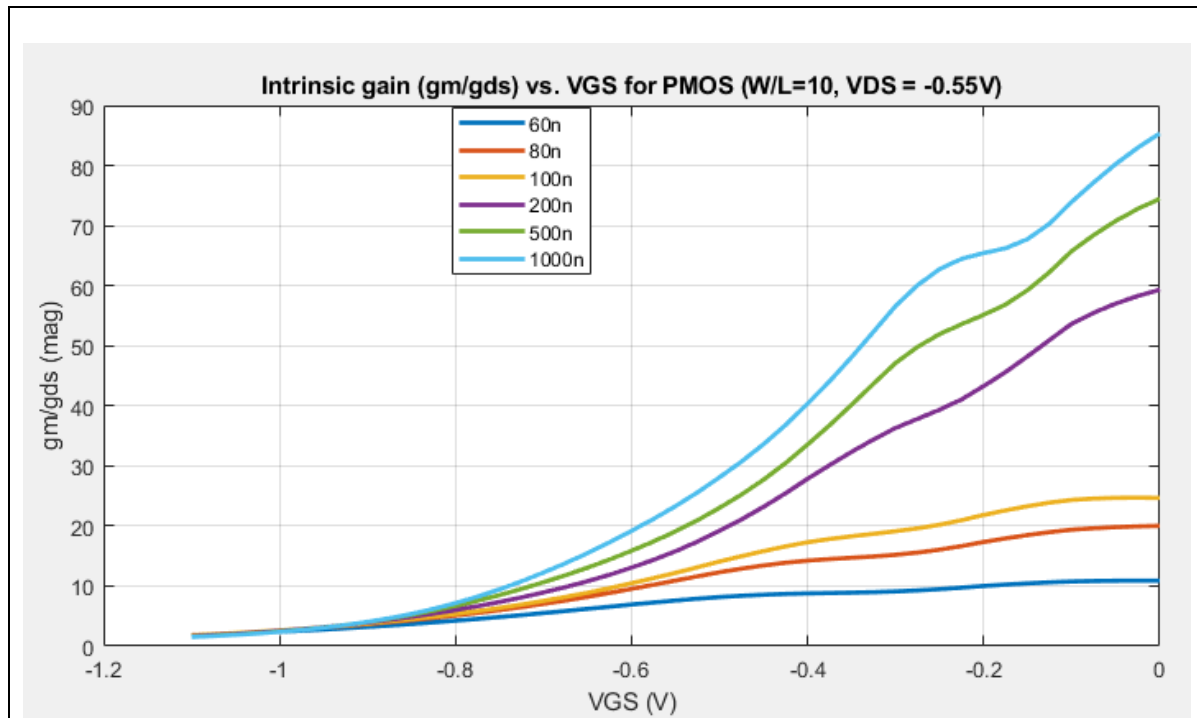


Fig.2

Figure 2:  $\frac{g_m}{g_{ds}}$  vs  $V_{GS}$  across gatelength  $L$

 


Fig. 3

Figure 3:  $\frac{g_m}{g_{ds}}$  vs  $V_{OV}$  across gatelength  $L$

 


Fig. 4

Figure 4:  $\frac{g_m}{g_{ds}}$  vs  $V_{GS}$  across gatelength  $L$

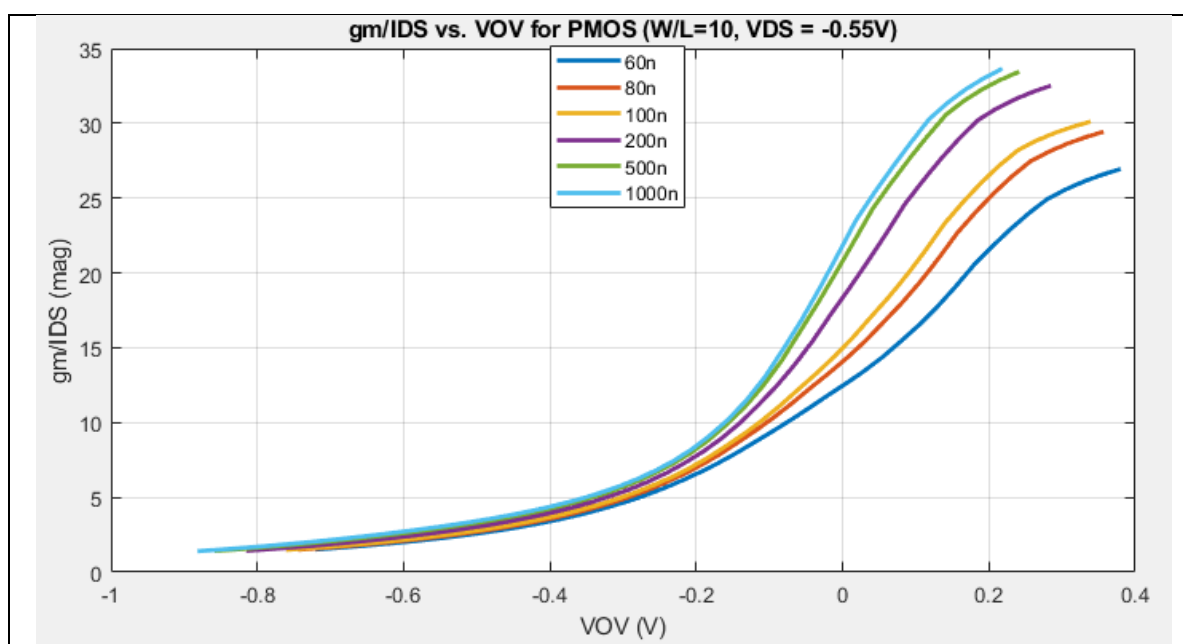


Fig. 5

Figure 5:  $\frac{g_m}{I_D}$  vs  $V_{OV}$  across gatelength  $L$

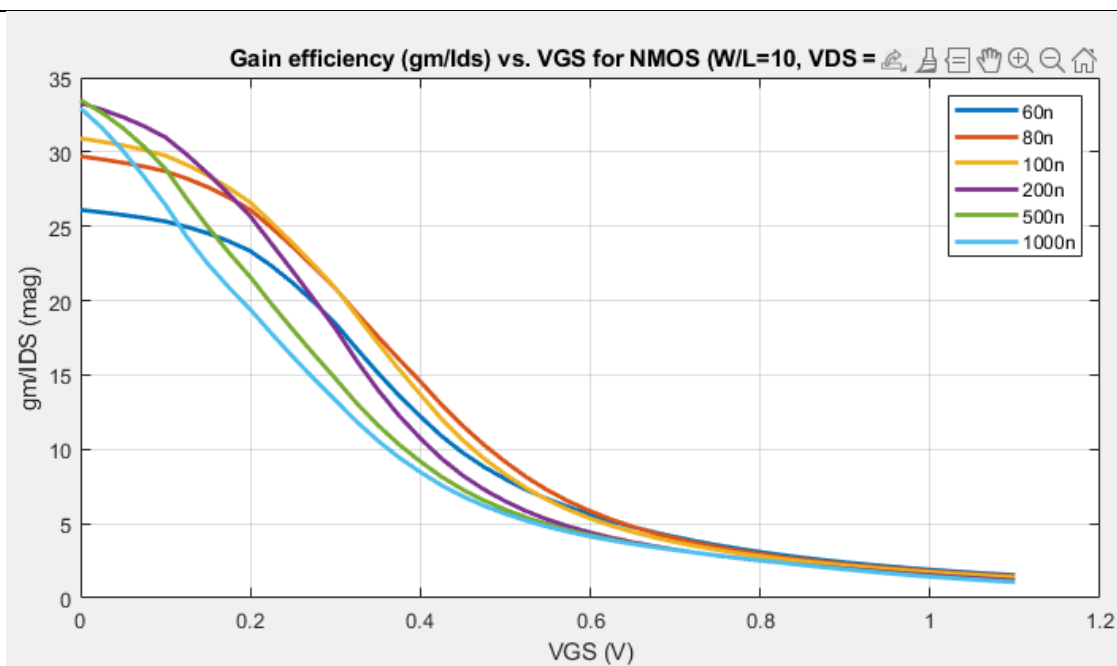


Fig.6

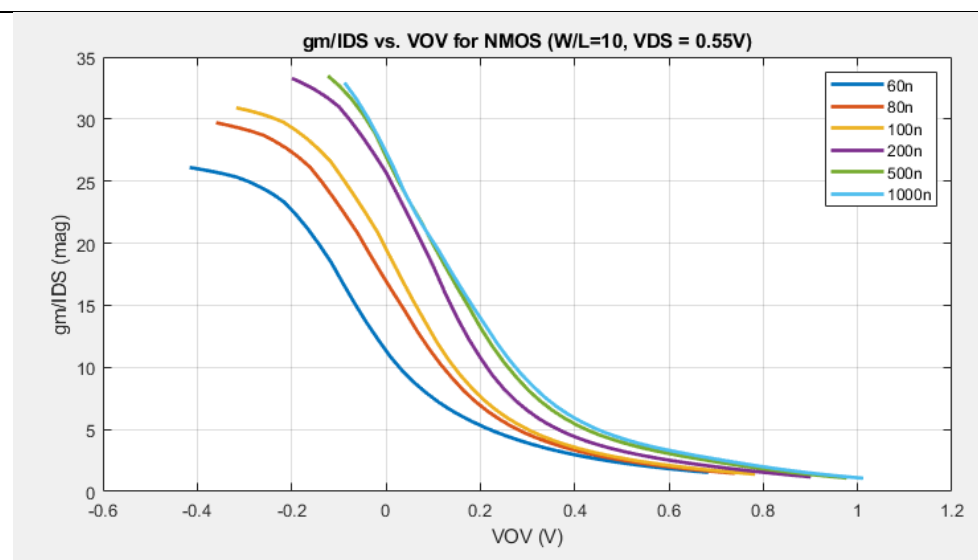


Fig. 7

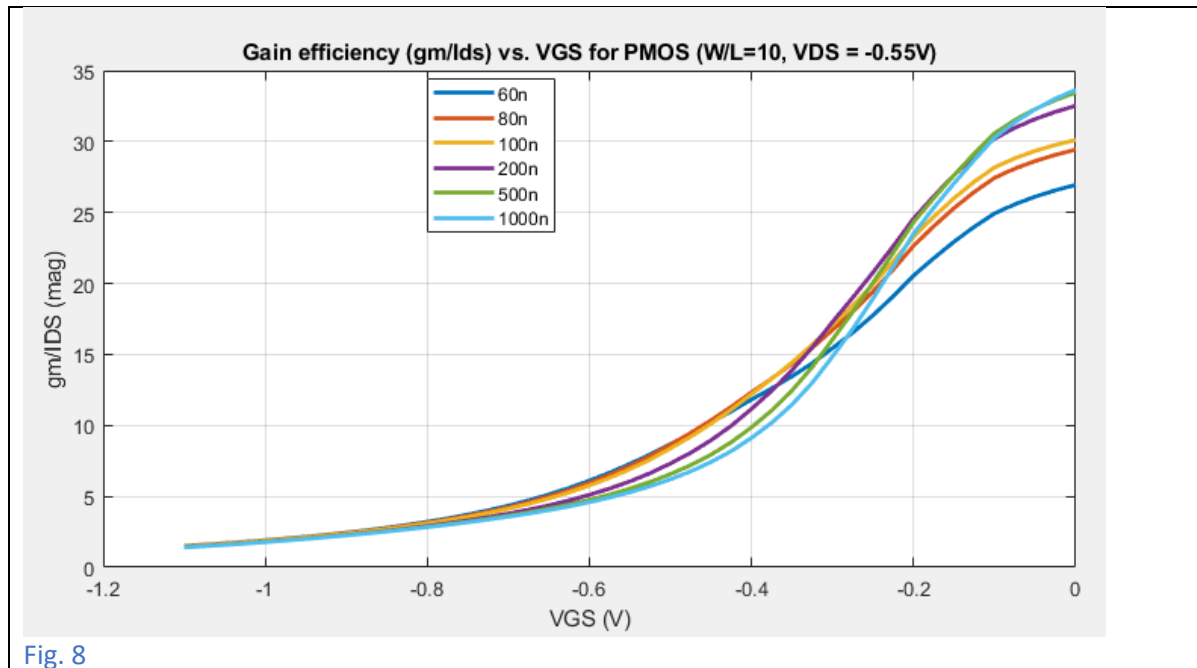


Fig. 8

#### Handcalculations:

Given Specifications:

$$C_L = 3\text{pF}$$

$$f_{GBW} = 50\text{MHz}$$

$$\text{DC gain} = 48\text{dB}$$

A necessary precaution is that zero compensation of the second pole and frequency gain bandwidth should be  $f_{2\text{nd pole}} \geq f_{GBW}$

$$C_M = \frac{1}{4} \cdot C_L = \frac{3\text{pF}}{4} = 0.75\text{pF}$$

Second pole approximation expression for a larger miller capacitance  $C_M$  and  $C_L$

$$f_{2\text{nd pole}} \approx gm_6 / (2\pi \cdot C_L)$$

I take  $gm_6 = n \cdot gm_1$  where  $n=\text{slope}$  and it is  $1.5 \leq n \leq 5$ , I choose  $n=1.5$

$$gm_1 = f_{GBW} \cdot 2\pi \cdot C_M = 50\text{e6} \times 2\pi \times 0.75\text{e-12} = 2.3565\text{e-4S} = 0.23565\text{mA/V}$$

$$\text{For stability: } -\frac{gm_6}{C_L} \approx n \cdot f_{GBW}. \text{ Hence, } gm_6 = n \cdot \frac{C_L}{C_M} \cdot gm_1 = 1.5 \times \frac{3 \times 10^{-12}}{0.75 \times 10^{-12}} \times 0.23565\text{e-4} = 1.4139 \times 10^{-3} = 1.4139\text{mA/V}$$

To maximize the voltage swing while the input stage transistors are kept in saturation,  $V_{DS6} = \frac{V_{DD}}{2} = 0.55\text{V} = 550\text{mV}$

To find the values of  $i_{ds,6}$ ,  $g_{ds,6}$  and  $v_{gs,6}$  look the graphs

DC Voltage gain= Stage1DC gain  $\times$  Stage2 DC gain

$$\begin{aligned} &= \frac{gm_2}{g_{ds2} + g_{ds4}} \times \frac{gm_6}{g_{ds6} + g_{ds5}} = A_{VDC1} \times A_{VDC2} \\ &\approx \frac{1}{2} \frac{gm_2}{g_{ds2}} \times \frac{gm_6}{g_{ds6}} \quad (g_{ds5} \ll g_{ds6}) \text{ and } g_{ds4} \approx g_{ds2} \end{aligned}$$

Check the graph of  $gm_1/g_{ds1}$  at  $L_1=200\text{nm}$ ,  $V_{ov}=0.1\text{V}$ , I obtained 45.6328,  $g_{ds1}=5.16404 \times 10^{-6}$

Note:  $\frac{g_{m1}}{g_{ds1}} = \frac{2.3565 \times 10^{-4}}{5.16404 \times 10^{-6}} = 33.18 \text{ dB}$  (Mp1 is symmetry with MP2)

For  $I_{DS1}$ , from fig.6, the graph of  $g_m/I_{DS} = 26.1603 \text{ V}^{-1}$  at  $V_{OV} = 0.1 \text{ V}$ ,  $L_1 = 200 \text{ nm}$ ,  $g_{m1}$  is already known,  $I_{DS1} = 9.0079 \times 10^{-6} = 9 \mu\text{A}$

The values are the same for transistor 2,  $M_{P2}$  by symmetry.

$$M_{n6}$$

Starting the sizing of the transistor from the output  $M_{n6}$  on the specification because I want a small intrinsic gain ( $\frac{g_{m6}}{g_{d6}}$ ) I chose  $L_6 = 80 \text{ nm}$  so that most of the gains will be made at the first stage of the circuit and avoid short channel modulation effects, the length should not be too short. I choose a weak inversion level for economical circuit design  $V_{OV6} = 0 \text{ V}$ , the lower the  $V_{ov}$  the better the cost.

For current mirror,  $V_{GS4} = V_{DS4} = V_{GS3}$  and  $V_{GS6} = V_{DS3}$

Fig. 7,  $g_{m6}/I_{D6}$  at  $V_{ov}=0\text{V}$ , with  $L_6=80\text{nm}$  I obtained 16.0516, therefore,  $I_{DS6}=8.808 \times -5\text{A}$ .

From graph  $g_m/g_{ds}$  at  $V_{ov,6}=0\text{V}$ , I obtained 16.4227, the  $g_{ds6}=8.609 \times 10^{-5} \text{ S}$

$$M_{n3} \text{ and } M_{n4} (\text{Symmetry})$$

For  $g_{m3}$ , from the fig. 7,  $g_{m3}/I_{DS3}$  at  $V_{OV} = 0.16$  (obtained from Matlab) with  $L_3=200\text{nm}$ , which is 14.004,  $I_{DS3} = I_{DS1} = 9.0079 \times 10^{-6} \text{ A}$ . To obtain a high gain in the first stage I increase the channel length of the transistor and work in weak inversion to have a low  $g_{ds3}$ .

I obtained  $g_{m3} = 1.261 \times 10^{-4} \text{ S}$ . According to fig. 3,  $g_{m3} / g_{ds3} = 38.157$ ,  $g_{ds3} = 3.3048 \times 10^{-6} \text{ S}$ .

$$M_{P5}, M_{P7}, M_{P8}$$

For  $g_{m5}$ , I use fig. 5,  $g_m/I_{DS} = 8.19077$  at  $V_{OV} = -0.2 \text{ V}$ , with  $L_5 = 1000 \text{ nm}$   $I_{DS} =$

$I_{DS6} = I_{DS5} = 8.808 \text{ e} - 5 \text{ A}$  also  $|V_{DS5}| = V_{DD} - V_{DS6} = 0.55 \text{ V}$ .

$g_{m5} \Rightarrow 7.2144 \text{ e} - 04 \text{ S}$

$V_{DSAT6} \leq V_{out} \leq V_{DD} - |V_{DSAT,5}|$  which means I need a small  $|V_{DSAT,5}|$  which is a weak inversion regime

To find  $g_{ds,5}$ , use fig.1,  $g_{m5}/g_{ds5} = 36.8236$  at  $V_{OV,5} = -0.2$ , I obtained  $g_{ds,5} = 1.9592 \text{ e} - 05 \text{ S}$

For transistor 7, I choose  $V_{DS7} = -0.25$ ,  $V_{D7} = V_{S1} = 1.1 - 0.25 = 0.85 \text{ V}$ . Increasing the channel length of  $M_{P7}$  will allow it to function as a good current source, so I choose  $L_7 = 1000 \text{ nm}$  (good current source) where  $V_{in} < V_{DD} + V_{ov,7} + V_{GS,1}$ , to obtain a high input common mode range, the  $V_{ov7}$  is kept low using low inversion regime  $V_{OV} = -0.2 \text{ V}$ .

Because the gate and drain of  $M_{P8}$ , also  $M_{P7}$  and  $M_{P8}$  have  $L_7 = L_8 = L_5$  to better control the current ratio between them.

$V_{GS,5} = V_{DS,8} = V_{GS7} = V_{DS,8}$ , I found the  $V_{ov7}$ ,  $V_{ov8}$  from fig.1.

This gives  $I_{DS7} = 2 * I_{DS1} = 2(9.0079 \times 10^{-6} \text{ A}) = 1.801 \times 10^{-5} \text{ A}$

DC Voltage gain = Stage 1 gain  $\times$  Stage 2 gain

$$\begin{aligned} &= \frac{g_{m2}}{g_{ds2} + g_{ds4}} \times \frac{g_{m6}}{g_{ds6} + g_{ds5}} = A_{VDC1} \times A_{VDC2} = \\ &\approx \frac{1}{2} \frac{g_{m2}}{g_{ds2}} \times \frac{g_{m6}}{g_{ds6}} \quad (g_{ds5} \ll g_{ds6}) \text{ and } g_{ds4} \approx g_{ds2} \end{aligned}$$

$$g_{ds2} = g_{o2} = g_{ds1} = 5.164 \times 10^{-6} S$$

$$g_{ds4} = g_{o4} = g_{ds3} = 3.3048 \times 10^{-6} S$$

$$g_{ds5} = g_{o5} = 1.9592 \times 10^{-5} S$$

$$g_{ds6} = g_{o6} = 8.609 \times 10^{-5} S$$

$$g_{m2} = g_{m1} = 235.65 \mu S$$

$$g_{m6} = 1413.9 \mu S$$

$$A_{V1} = g_{m1}/g_{o4} + g_{o2} = 27.83$$

$$A_{V2} = g_{m6}/g_{o5} + g_{o6} = 13.38$$

$$DC \text{ gain} = A_{V(TOTAL)} = A_{V1} \times A_{V2} = 372.33$$

$$AV[dB] = 20 \log(AV) = 51.4 dB$$

$$\text{Node 1; } w_{p1} = \frac{g_{m3}}{C_{n1}}; w_{z1} = 2 * \frac{g_{m4}}{C_{n1}}$$

$$\text{Node 2: } w_{p2} = \frac{g_{ds1} + g_{ds3}}{C_M(1 + A_{V2})}; w_{z2} = \frac{1}{C_M(\frac{1}{g_{m6}} - R_M)}$$

To compensate for non-dominant pole, I used the formula,

$$R_M = \frac{C_L}{C_M * g_{m6}} + \frac{1}{g_{m6}} = \frac{C_L}{C_M * g_{m6}} + \frac{1}{1413 \times 10^{-6} S} = \frac{3 pF}{0.75 pF \times 1.4139 \times 10^{-3}} + 707.2635 = 3.5363 k\Omega$$

$R_M$  is such that the pole on node 3 is compensated by zero on node 2, which means  $w_{p3} = w_{z2}$

$$\text{The dominant pole frequency} = w_{p2} = P_{dom} = \frac{f_{GBW}}{A_{V(TOTAL)}} = \frac{50 MHz}{51.4 dB} = 134.4086 \text{ kHz} =$$

$$\text{Rather, } P_{dom} = \frac{f_{GBW}}{A_{V(TOTAL)}} = 2\pi \times 50 \times \frac{10^6}{372.33} = 0.84388 MHz$$

$$\text{Total Phase Shift} = 0^\circ - \arctan \frac{f_{GBW}}{P_{dom}} = 0^\circ - \arctan \left( \frac{50 MHz}{134.33 KHz} \right) = -89.84^\circ$$

Adding  $w_{z2}$  to PM I obtain, Phase Margin:


$$PM = \text{Total Phase Shift} - (-180^\circ) = -89.88^\circ + 180^\circ = 90.15^\circ$$

$$\text{Node 3: } w_{p3} = \frac{g_{m6}}{C_L} = \frac{1.4139 \times 10^{-3} S}{3 pF}$$



- 2) Place all the calculated voltages (in the blackbox) and all currents (in the red box) on the circuit depicted below and calculate also:

$V_{cm,in,min}$	$V_{gs3} - V_{dsat1} + V_{gs1} = 115.4mV$
$V_{cm,in,max}$	$V_{DD} - V_{gs1} - V_{ov} = 736.4mV$
$V_{out,min}$	$V_{dsat,6} = 62.91mV$
$V_{out,max}$	$V_{DD} +  V_{dsat,5}  = 914.4mV$
$P_{diss}$	$V_{DD} (I_{ds} + I_{ds,7} + I_{ds,8}) = 0.1mW$

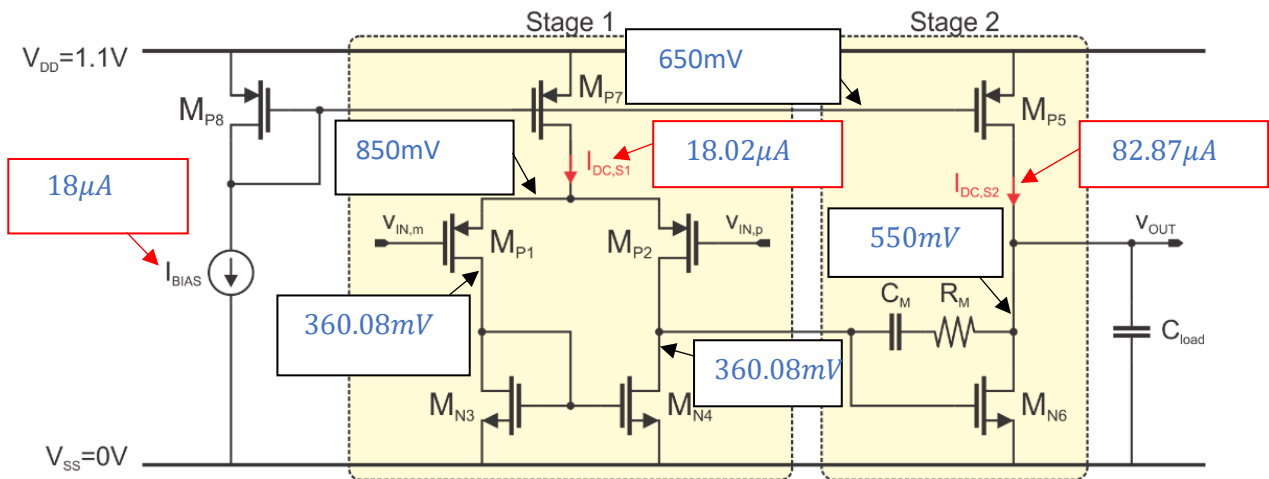

**Design: Implementation of the OpAmp in MATLAB and LTspice (10 points):**

- 3) Based on your handcalculations, create your OpAmp design in MATLAB. After completion, please insert your final and entire MATLAB code after the appendix (i.e. at the end of this report-document).

Remark:

- Please make sure that all widths  $W$  are below 1mm

- 4) Fill out both tables depicted below. All values are to be determined in MATLAB.

Device sizes and bias point parameters according to MATLAB

Device	W [ $\mu\text{m}$ ]	L [nm]	$I_{ds}$ [ $\mu\text{A}$ ]	$V_{ov}$ [V]	$g_m$ [S]	$g_{ds}$ [S]	$g_m/g_{ds}$ [-]	$V_{ds,sat}$ [V]	$V_{ds}$ [V]
$M_{p1}$	55.47	200	9.25	100.00m	235.62 $\mu$	5.28 $\mu$	44.625	-44.56m	-550.00m
$M_{p2}$	55.47	200	9.25	100.00m	235.62 $\mu$	5.28 $\mu$	44.625	-44.56m	-550.00m
$M_{n3}$	0.481	200	9.25	162.32m	125.40 $\mu$	4.50 $\mu$		115.56m	360.08m
$M_{n4}$	0.481	200	9.25	162.32m	125.40 $\mu$	4.50 $\mu$		115.56m	360.08m
$M_{p5}$	26.94	1000	82.87	-200.00m		18.50 $\mu$		-175.21m	-550.00m
$M_{n6}$	6.86	80	82.87	-1.46u	1.410m	86.46 $\mu$	16.308	63.11m	550.00m
$M_{p7}$	7.28	1000	18.47	-203.25m		33.17 $\mu$		-177.77m	-189.92m
$M_{p8}$	6.21	1000	18.49	-201.23m		5.61 $\mu$		-176.18m	-418.19m

Device	Units	Value
$C_M$	pF	0.750
$R_M$	$\Omega$	3536.3
$I_{BIAS}$	A	18.02 $\mu$

- 5) Based on the parameters filled in the table above, design your OpAmp in LTspice. After completion, please insert your final and entire LTspice-netlist after the appendix (i.e. at the end of this report-document).

**Experiment (10 points):**

In this section you will simulate the following:

- A. Frequency Response in MATLAB and LTspice
- B. Noise contribution in LTspice
- C. Linearity in LTspice

**Note on how to present graphs in general:**

- *When you make a graph, put labels on every axis to make clear what you are showing. Also, show the units!*
- *When you plot multiple curves on one graph, add a legend.*

#### A. Frequency Response in MATLAB and LTspice

*Note on how to present graphs in this sub-section:*


- For magnitude plots use dB (linear scale) vs. Hz (logarithmic scale)
- for phase plots use ° (linear scale) vs. Hz (logarithmic scale).

- 6) Simulate  $A_v$  (small voltage gain) with  $C_M$  and  $R_M$  in MATLAB and LTspice. Then, paste both  $A_v$ -curves in separate plots below such that the difference between MATLAB and LTspice can be clearly seen. In addition to that, indicate the resulting phase margin (PM) in both plots.

#### Plots:

Simulator	PM (deg)
MATLAB	86.7
LTspice	89.5

 - 7) Explain, analyse and interpret the results in “6)”. Furthermore, if you observe significant differences between MATLAB and LTspice, explain why.





8) Simulate  $A_v$  in LTspice for the following cases:

- No compensation network ( $C_M = R_M = 0$ ).
- With compensation capacitor but no compensation resistor ( $R_M = 0$ ).
- With both the compensation capacitor and the compensation resistor.

Then, show all 3 cases in separate plots such that the differences are clearly visible. Furthermore, indicate on each plot the resulting PM.

**Plot:**


### A. No compensation Network( $C_M = R_M = 0$ )



### B. With Compensation Capacitor but no compensation Resistor ( $R_M = 0$ )


 
### C. With both the compensation capacitor and the compensation resistor



There is a slight difference of  $8.4^\circ$  between the MATLAB PM ( $86.7^\circ$ ) and LT Spice ( $89.5^\circ$ ) because all the capacitances are not considered in MATLAB according to my hand calculations, the increase in PM in LTSpice is based on the frequency of the dominant pole which is smaller than that of the frequency of the dominant pole in MATLAB.

In MATLAB simulation, the zero is placed in the right hand half plane at the non-dominant pole frequency to compensate the non-dominant pole which helped in achieving the obtained PM, two poles and one zeros.

Therefore, the LT Spice and MATLAB use difference database, for example the difference in  $V_{th}$  and  $V_{ov}$  in the two softwares

Case	PM [deg]
No compensation network	$180-178= 2$
No compensation resistor	$180-125= 54.7$
With both the compensation	$180-90.2=89.5$

9) Explain, analyse and interpret the results in “8”).

Case A. When there is no RM and CM, the PM decreases a lot, the GBW also becomes larger. The dominant and non-dominant poles both shifted to higher frequencies (299.5MHz), which means the circuit may face instability and be greatly perturbed by  $C_{load}$  adding its effects around the cross over

frequency which reduces the PM because the two poles are also close to the cross over frequency.

Case B. With Compensation Capacitor but no compensation Resistor ( $R_M = 0$ ), the compensation capacitor ( $C_M = 0.75$ ) explores the effect of miller capacitance by causing pole splitting, moves the pole of the  $C_{load}$  (non-dominant pole) away to higher frequency than the cross frequency. The non-dominant pole and the positive zero induce  $90^\circ$  phase shift each, the value of the zero is high to have effect on the PM. The dominant pole is moved to a lower frequency (41.04MHz), this improves the PM ( $54.7^\circ$ ).

Case C: With both the compensation capacitor and the compensation resistor, the  $R_M$  added allows the positive zero  $Z_2$  to be moved to lower frequency at the left half plane, the  $z_2$  helps in compensating the non dominant pole ( $P_3$ ) with absolute value close to the cross over frequency. This results in an increase PM where it is mostly needed. The unity gain frequency also increase because there is no more non-dominant pole.



## B. Noise contribution in LTspice

- 10) Simulate the output-referred noise voltage power density  $\overline{dv_{out,eq}^2}/\Delta f$  over an appropriate frequency range in LTspice. Then, insert the  $\overline{dv_{out,eq}^2}/\Delta f$ -plot below.

### Plots:



- 11) Explain, analyse and interpret the results in “10”.


I plotted the graph until  $10 \cdot f_{GBW}$  which corresponds to the DC gain I obtained approximately, in the plot of output-referred noise voltage power density decreases exponentially until  $0 \text{ dB } (v^2/\text{Hz})$  in logarithmic scale, as the frequency increases towards  $(10 \times 48.44 \text{ MHz})$ . This is the characteristics of flicker noise which depends on  $1/f$ . The noise decreases stronger as the gain is attenuated which add further to the flicker noise. At around  $23 \text{ MHz}$ , slope begins to change which corresponds to white noise (thermal noise) which is directly proportional to the frequency.

- 12) Simulate the input-referred noise spectral density by using the .NOISE option in LTspice. Also, by using LTspice, determine the total output integrated noise of the OpAmp. For that, take the integration bandwidth from  $10 \text{ kHz}$  to  $10 \cdot f_{GBW}$ . Furthermore, copy and paste the top 9 contributing elements using "View->SPICE Error Log" option and insert that list below.

out\_totnvrms: INTEG(v(onoise))=0.00470396 FROM 1000 TO  $8e+10$

out\_mp1nvrms: INTEG(v(mp1))=0.00165599 FROM 1000 TO  $8e+10$

out\_mp2nvrms:  $\text{INTEG}(v(\text{mp2}))=0.00165923$  FROM 1000 TO  $8e+10$   
 out\_mp7nvrms:  $\text{INTEG}(v(\text{mp7}))=6.81114e-05$  FROM 1000 TO  $8e+10$   
 out\_mp8nvrms:  $\text{INTEG}(v(\text{mp8}))=3.02047e-05$  FROM 1000 TO  $8e+10$   
 out\_mp5nvrms:  $\text{INTEG}(v(\text{mp5}))=3.74476e-05$  FROM 1000 TO  $8e+10$   
 out\_mn6nvrms:  $\text{INTEG}(v(\text{mn6}))=9.59835e-05$  FROM 1000 TO  $8e+10$   
 out\_mn4nvrms:  $\text{INTEG}(v(\text{mn4}))=0.00299437$  FROM 1000 TO  $8e+10$   
 out\_mn3nvrms:  $\text{INTEG}(v(\text{mn3}))=0.00276476$  FROM 1000 TO  $8e+10$   
 out\_rmnvrms:  $\text{INTEG}(v(\text{rm}))=7.35347e-05$  FROM 1000 TO  $8e+10$

 


13) Explain, analyse and interpret the results in “12”.

The OTA's total output integrated RMS noise is measured to be **0.00470396  $V_{rms}$** . At the first stage, the major contributors to the overall noise are Mp1, Mp2, mp3, and MP4. This noise is further amplified by the second stage. On the other hand, the noise contribution of MN6 and MP5 is reduced because they are not amplified by the second stage. MP7, MP8, and MP5, which function as current mirrors, exhibit significantly lower noise contributions since they are not amplified. They have longer gate lengths and are evenly distributed across the two branches of the OTA circuit, generating a common-mode contribution that is rejected by the OTA's common-mode rejection.


In the graph, there is an initial low-frequency region corresponding to flicker noise, followed by a flat region indicating white noise. The flicker noise, which exhibits a  $1/f$  dependency, is inversely proportional to the

transistor area, as observed in the graph. As the frequency increases, there is a slight increase in noise due to the decreasing gain for input-referred RMS noise, causing the noise spectral density to be divided by a diminishing gain

 The Voltage gain and Output Voltage Amplitude as a function of the Input Voltage amplitude



 Frequency (Hz) response of the amplitude and Voltage gain as a function of the input voltage amplitude.




C. Linearity in LTspice

- 14) Simulate the output voltage amplitude and voltage gain as a function of the input voltage amplitude in LTspice. Then, insert the plots below and indicate the 1-dB compression point.

Plots:

Vin (V)	Vin (dBvrms)	Vout (dBvrms)	Gain (dB)
0.000001	-123.0	-70.208356	52.8
2.1544E-06	-116.3	-66.2	50.1
4.6415E-06	-109.7	-59.6	50.1
0.00001	-103.0	-52.4	50.6
2.1544E-05	-96.3	-45.2	51.1
4.6415E-05	-89.7	-39.1	50.6
0.0001	-83.0	-32.7	50.3
0.00021544	-76.3	-26.2	50.1
0.00046415	-69.7	-19.9	49.8
0.001	-63.0	-14.5	48.5
0.0021544	-56.3	-10.6	45.7
0.0046415	-49.7	-9.6	40.1
0.01	-43.0	-9.6	33.4
0.021544	-36.3	-8.1	28.2
0.046415	-29.7	-8.6	21.1
0.1	-23.0	-7.9	15.1

 

15) Explain, analyse and interpret the results in "14)".

There are two saturation points observed which are 0V and 1.1V (VDD) which creates non-linearity that causes the sine wave to be compressed as the voltage keeps increasing it turns the waveform to become a square waveform preventing further increase in amplitude and reaching the saturation of the output voltage, at this time the first order linear coefficient  $K_1$  has a lot of effect on the fundamental tone output according to the relationship fundamental tone Output =  $K_1 A_1 + 3/4 K_3 A_1^3$ .

For graph B (the compression plot ( $V_{out} \times V_{in}$ ), 1-dB compression point is observed at -89.7dB with the input Voltage Amplitude value of  $4.6415 \times 10^{-05}$ . The linearity of the OTA for input signals with varying amplitudes, show a linearity at low  $V_{in}$  and becomes saturated at higher  $V_{in}$ .

For graph A (Gain x  $V_{in}$ ), the same behavior is noticeable with the gain that is very close to 48dB for low  $V_{in}$  while it begins to reduce for higher  $V_{in}$ .

### Conclusion (10 points):

16) Conclude your experiment by filling the editable fields in the performance table depicted below

Metric	Units	Specification	from hand-calculations	MATLAB	LTspice
DC gain	magnitude	251.2	295.1	231.7	264.2
DC gain	dB	48	49.4	47.3	48.4
Gain-Bandwidth frequency $f_{GBW}$	MHz	50	51	50.2	48.80
Dominant pole frequency $f_{dom}$	kHz	199	173	216.7	194.3
PM	°	> 70	90.1	86.7	89.5
$V_{in,cm,max} - V_{in,cm,min}$	V		0.61	0.622	0.318
$V_{out,max} - V_{out,min}$	V	> 0.7	0.85	0.862	0.856
$P_{diss}$	mW		0.13	0.1	0.14
$\overline{v_{out,eq}^2}$ (output-referred noise)	V <sub>rms</sub>				0.000457165

17) Comment about the deviations between hand calculation, MATLAB and LTspice values found above.  
Conclude, what the causes of such deviations are.

There is a slight difference of 8.4° between the MATLAB PM (86.7 °) and LT Spice (89.5°) because all the capacitances are not considered in MATLAB according to my hand calculations, the increase in PM in LT Spice is based on the frequency of the dominant pole which is smaller than that of the frequency of the dominant pole in MATLAB.

In MATLAB simulation, the zero is placed in the right hand half plane at the non-dominant pole frequency to compensate the non-dominant pole which helped in achieving the obtained PM, two poles and one zeros. Therefore, the LT Spice and MATLAB use difference database, for example the difference in  $V_{th}$  and  $V_{ov}$  in the two softwares

The value of the  $f_{dom}$  which is  $f_{dom} = f_{GBW} / (10^{(DCgain/20)})$  for handcalculation (173kHz) and Matlab (164kHz) are almost equal because their DC gain gain value are almost the same unlike LT spice (194kHz) that has a higher DC gain value.

18) If you have results which are not passing the specifications: conclude for each of those result what the cause is and what you need to do in order to make it pass, if you were repeating this experiment.

To conclude, my circuit has successfully passed all the requirements in MATLAB, hand calculation and LT Spice which includes, the width that is less than 1mm, all specifications error margin of 10% are all respected. The difference in the DC gain bandwidth could be due to the  $R_M$  and  $C_M$  values used which do not perfectly correlated.

The handcalculated  $R_m$  value worked both in LT spice and in the MATLAB.



## **Appendix:**

Insert your MATLAB code here:

```
% Analog Electronics final project
clc;
close all;
clear;

addpath(genpath('circuitDesign'));
addpath(genpath('functions'));
addpath(genpath('models'));

load('UMC65_RVT.mat');

%% Initializations
designkitName      = 'umc65';
circuitTitle      = 'Analog Design - Project';
elementList.nmos   = {'Mn3','Mn4','Mn6'};
elementList.pmos   = {'Mp1','Mp2','Mp5','Mp7','Mp8'};

choice.maxFingerWidth = 10e-6;
choice.minFingerWidth = 200e-9;

simulator          = 'spectre';
simulFile          = 0;
simulSkelFile      = 0;
spec               = [];
analog              = cirInit('analog',circuitTitle,'top',elementList,spec,choice,...

                                designkitName,NRVT,PRVT,simulator,simulFile,simulSkelFile);
analog              = cirCheckInChoice(analog, choice);

%% Project: circuit
disp(' ');
disp(' VDD      VDD      VDD      ');
disp(' |          |          |          ');
disp(' Mp8+-----Mp7-----Mp5      ');
disp(' |--+      |          |          ');
disp(' |      +---+---+ node 3-> +-----+OUT ');
disp(' |      |      |          |      ');
disp(' | IN1--Mp1 Mp2--IN2      |      ');
disp(' |      |      |          |      ');
disp(' | node 1-> |      | <-node 2      | Cl      ');
```

```

disp(' |      |--+ +-----+Cm---Rm-----+ |      ');
disp(' |bias  | | | |      ↑ | | |      ');
disp(' |      Mn3--+Mn4 | node 4 | |      ');
disp(' |      | |      +-----Mn6 | |      ');
disp(' |      | |      | |      ');
disp(' | GND      GND GND      GND GND      ');

```

%% AI: Implement your OpAmp according to your handcalculations

## % specifications

```
spec.VDD = 1.1;
```

```
spec.fGBW = 50e6; %MHz
```

```
spec.Cl = 3e-12; %pF
```

```
spec.GBW=spec.fGBW*(2*pi);
```

```
spec.gain = 48; %DB
```

$$\text{spec.Cm} = 0.25 * \text{spec.Cl}; \% \text{Cm} = 0.75 \text{pF}$$

```
spec.Rm = 3.5363e+3;
```

```
l_bias = 18e-6;
```

% Design Mn6

```
Mp1.gm = spec.fGBW * 2 * pi * spec.Cm;
```

 $n = 1.5;$ 
$$Mn6.gm = n * spec.Cl * Mp1.gm / spec.Cm;$$

Mn6.vds = 550e-3;

Mn6.vov = 0;

Mn6.lg = 80e-9;

Mn6.vsb = 0.0;

```
Mn6.vth = tableValueWref('vth', NRVT, Mn6.lg, 0, Mn6.vds, Mn6.vsb); % vgs still unknown
```

$$Mn6.vgs = Mn6.vth + Mn6.vov;$$

```
Mn6.w = mosWidth('gm', Mn6.gm, Mn6);
```

```
Mn6 = mosNfingers(Mn6);
```

```
Mn6 = mosOpValues(Mn6);
```

% design Mp5

Mp5.ids = Mn6.ids;

```
Mp5.vsb = 0;
```

Mp5.lg = 1000e-9;

Mp5.vov = -0.2;

```
Mp5.vds = -(spec.VDD - Mn6.vds);
```

```
Mp5.vth = tableValueWref('vth', PRVT, Mp5.lg, 0, Mp5.vds, Mp5.vsb);
```

$$M_{p5.vgs} = M_{p5.vth} + M_{p5.vov};$$

```
Mp5.w = mosWidth('ids', Mp5.ids, Mp5);
Mp5 = mosNfingers(Mp5);
Mp5 = mosOpValues(Mp5);

% design Mp1 and Mp2

Mp1.vds = -spec.VDD / 2;
Mp1.vsb = 0;
Mp1.vov = 0.1;
Mp1.lg = 200e-9;
Mp1.vth = tableValueWref('vth', PRVT, Mp1.lg, 0, Mp1.vds, Mp1.vsb);
Mp1.vgs = Mp1.vth + Mp1.vov;

% Mp2.ids = Mp1.ids;
Mp1.w = mosWidth('gm', Mp1.gm, Mp1);
Mp1 = mosNfingers(Mp1);
Mp1 = mosOpValues(Mp1);

Mp2 = cirElementCopy(Mp1,Mp2);

% design Mn3 and Mn4
Mn3.ids = Mp1.ids;
Mn3.vds = Mn6.vgs;
Mn3.vgs = Mn3.vds;
Mn3.vsb = 0;
Mn3.lg = 200e-9;

Mn3.vth = tableValueWref('vth', NRV, Mn3.lg, Mn3.vgs, Mn3.vds, Mn3.vsb);
Mn3.vov = Mn3.vgs - Mn3.vth;

Mn3.w = mosWidth('ids', Mn3.ids, Mn3);
Mn3 = mosNfingers(Mn3);
Mn3 = mosOpValues(Mn3);

Mn4 = cirElementCopy(Mn3, Mn4);

% design Mp7

Mp7.vds = -(spec.VDD + Mp1.vds - Mn3.vds);
Mp7.lg = 1000e-9;
Mp7.ids = 2 * Mp1.ids;
Mp7.vsb = 0;
Mp7.vgs = Mp5.vgs;

Mp7.vth = tableValueWref('vth', PRVT, Mp7.lg, Mp7.vgs, Mp7.vds, Mp7.vsb);
```

```
Mp7.vov = Mp7.vgs - Mp7.vth;
```

```
Mp7.w = mosWidth('ids', Mp7.ids, Mp7);
```

```
Mp7 = mosNfingers(Mp7);
```

```
Mp7 = mosOpValues(Mp7);
```

```
% design Mp8
```

```
Mp8.vgs = Mp7.vgs;
```

```
Mp8.vds = Mp8.vgs;
```

```
Mp8.lg = Mp7.lg;
```

```
Mp8.ids = Mp7.ids; % = I_bias
```

```
Mp8.vsb = 0;
```

```
Mp8.vth = tableValueWref('vth', PRVT, Mp8.lg, Mp8.vgs, Mp8.vds, Mp8.vsb);
```

```
Mp8.vov = Mp8.vgs-Mp8.vth;
```

```
Mp8.w = mosWidth('ids', Mp8.ids, Mp8);
```

```
Mp8 = mosNfingers(Mp8);
```

```
Mp8 = mosOpValues(Mp8);
```

```
Av_TotalGain_dB = db(Mp1.gm * Mn6.gm / (Mp1.gds + Mn4.gds) / (Mn6.gds + Mp5.gds));
```

```
%% AI: Fill out the empty variables required to plot the transfer-function.
```

```
% meaning of each variable see comment and
```

```
% location of nodes see line 31
```

```
AvDC1 = Mp1.gm / (Mp1.gds + Mn4.gds); % DC gain 1st stage
```

```
AvDC2 = Mn6.gm / (Mn6.gds + Mp5.gds); % DC gain 2nd stage
```

```
AvDC1dB = 20*log10(AvDC1); % DC gain 1st stage [dB]
```

```
AvDC2dB = 20*log10(AvDC2); % DC gain 2nd stage [dB]
```

```
Av_Total=AvDC1*AvDC2;
```

```
C1 = Mp1.cgd + Mp1.cgs + Mn4.cgs; % Capacitance on node 1
```

```
G1 = Mn3.gm; % Admittance on node 1
```

```
C2 = spec.Cm*(1+AvDC2); % Capacitance on node 2
```

```
G2 = Mp2.gds + Mn4.gds; % Admittance on node 2
```

```
C3 = spec.Cl; % Spec.Cl + spec.Cm; % Capacitance on node 3
```

```
G3 = Mn6.gm; % Admittance on node 3
```

```
C4=Mn6.cgs + Mn6.cgd;
```

```
p3 = G3/C3;
```

```
G4 = 1/(spec.Rm) + Mn6.gm;
```

```
%% AI: Set-up Rm, Cc and Cl and calculate the zero required for the transfer-fct
```

```
z1 = 1/((1/Mn6.gm - spec.Rm) * spec.Cm);
```

```
%% AI: Fill out the empty variables required for the performance summary
```

```

Vin_cm_min = Mn3.vdsat;
Vin_cm_max = spec.VDD + Mp7.vdsat + Mp1.vgs;
Vout_cm_min = Mn6.vdsat;
Vout_cm_max = spec.VDD + Mp5.vdsat;
Pdisss    = spec.VDD * (Mp8.ids + Mp7.ids + Mp5.ids);

%% Sanity check (do not modify)

disp('=====');
disp('=   Transistors in saturation   =');
disp('=====');
if mosCheckSaturation(Mp1)
    fprintf("\nMp1:Success\n")
end
if mosCheckSaturation(Mp2)
    fprintf('Mp2:Success\n')
end
if mosCheckSaturation(Mn3)
    fprintf('Mn3:Success\n')
end
if mosCheckSaturation(Mn4)
    fprintf('Mn4:Success\n')
end
if mosCheckSaturation(Mp5)
    fprintf('Mp5:Success\n')
end
if mosCheckSaturation(Mn6)
    fprintf('Mn6:Success\n')
end
if mosCheckSaturation(Mp7)
    fprintf('Mp7:Success\n')
end
if mosCheckSaturation(Mp8)
    fprintf('Mp8:Success\n\n')
end

%% Summary of sizes and biasing points (do not modify)

disp('=====');
disp('=   Sizes and operating points   =');
disp('=====');
analog = cirElementsCheckOut(analog); % Update circuit file with

% transistor sizes
mosPrintSizesAndOpInfo(1,analog); % Print the sizes of the

```

---

```
% Mp8.ids=1.8016e-05;
% transistors in the circuit file
fprintf('I_bias\t= %6.2f mA\nRm\t= %6.2f Ohm\nCm\t= %6.2f F\n\n',Mp8.ids/1e-3,spec.Rm,spec.Cm/1e-12);
% I_bias =18e-6;
spec.Cl = 3e-12;
omega_pdom = (spec.GBW)/Av_Total; % Desired dominant pole
Cm_Ideal = (Mp2.gds + Mn4.gds)/(omega_pdom * (1+AvDC2));
Rm_ideal = (1+ spec.Cl/Cm_Ideal)*(1/Mn6.gm);

poles = [G1/C1, G2/C2, G3/C3, G4/C4];
p1=G1/C1;
p2=G2/C1;
p3=G3/C3;
p4=G4/C4;

z2=2*p1;
zeros = [G1/C1/2, z1];
% if abs(p2) <abs(p3)
%   fGBW=Av_Total*p2/(2*pi);
% else
%   fGBW=Av_Total *p3/(2*pi);
% end

%% Performance summary (do not modify)

disp('=====');
disp('=      Performance      =');
disp('=====');

fprintf('\nmetrik      \t result\n');
fprintf('Vin,cm,min [mV] \t%.0f\n',Vin_cm_min/1e-3);
fprintf('Vin,cm,max [mV] \t%.0f\n',Vin_cm_max/1e-3);
fprintf('Vout,cm,min [mV] \t%.0f\n',Vout_cm_min/1e-3);
fprintf('Vout,cm,max [mV] \t%.0f\n',Vout_cm_max/1e-3);
fprintf('Pdiss [mW]      \t%.1f\n',Pdiss/1e-3);

%% Ploting transfer function (do not modify)

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% if control toolbox in Matlab is available
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

s = tf('s');
% transfer function
TF1 = AvDC1*AvDC2*((1+s*C1/(2*G1))*(1-s*(1/z1)))/ ...
```

$$((1+s*C1/G1)*(1+s*C2/G2)*(1+s*C3/G3)*(1+s*C4/G4));$$

```
freq = logspace(1,12,1e3);
figure(1)
margin(TF1,2*pi*freq); grid on;
h = gcr;
setoptions(h,'FreqUnits','Hz');
title('Frequency response Opamp');
hold all
```

Insert your LTspice netlist here:

```
vcm N006 0 0.65

E1 vinn N006 N006 vinp 1

V1 vinp N006 SINE(0 100u 1k) AC 10m

Mp8 N002 N002 N001 N001 p_11_sprvt l=1u w=6.86u

Mp7 N003 N002 N001 N001 p_11_sprvt l=1u w=7.28u

Mp1 N005 vinn N003 N003 p_11_sprvt l=200n w=55.47u

Mp2 vinter vinp N003 N003 p_11_sprvt l=200n w=55.47u

Mn4 vinter N005 0 0 n_11_sprvt l=200n w=0.481u

Mn3 N005 N005 0 0 n_11_sprvt l=200n w=0.481u

Mn6 vout vinter 0 0 n_11_sprvt l=80n w=6.86u

Mp5 vout N002 N001 N001 p_11_sprvt l=1u w=26.94u

Rm vout N004 3536

Cm N004 vinter 0.75p

Ibias N002 0 18u

Cload vout 0 3p

.model NMOS NMOS

.model PMOS PMOS

.lib C:\Users\Shola\AppData\Local\LTspice\lib\cmp\standard.mos
```

.lib BSIM4\_UMC65.lib

.noise V(vout) V1 dec 20 1k 80G

.meas NOISE out\_totnVrms INTEG V(onoise)

.meas NOISE out\_mp1nVrms INTEG V(mp1)

.meas NOISE out\_mp2nVrms INTEG V(mp2)

.meas NOISE out\_mp7nVrms INTEG V(mp7)

.meas NOISE out\_mp8nVrms INTEG V(mp8)

.meas NOISE out\_mp5nVrms INTEG V(mp5)

.meas NOISE out\_mn6nVrms INTEG V(mn6)

.meas NOISE out\_mn4nVrms INTEG V(mn4)

.meas NOISE out\_mn3nVrms INTEG V(mn3)

.meas NOISE out\_rmnVrms INTEG V(rm)

\* RMS total noise calculated at the output

\* RMS noise contribution from each element seen at the output

.backanno

.end